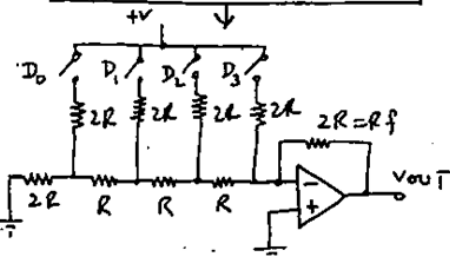


## Digital to Analog Converter DAC

## Binary Weighted

## LADDER OR R/2R DAC




R/2R because of Resistor values

Ladder  $V_p$  network like ladder so

$$V_o = \frac{V_0 2^0 + V_1 2^1 + V_2 2^2 + \dots + V_n 2^n}{2^n - 1}$$

$n$  = no. of total  $V_p$   
(Millman's theorem)


## COUNTER TYPE ADC Block diagram

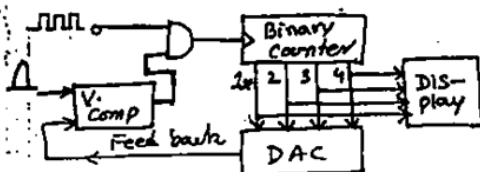

voltage comparator compare voltage with analog o/p of AND is clock of Binary counter will count at every clock & stop at  $O/P = Y_P$ .


## SUCCESSIVE APPROXIMATION ADC

Block diagram

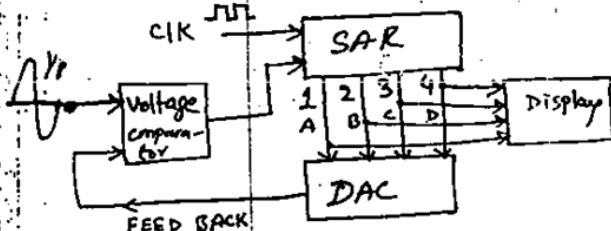

Falling Flow chart

Explain

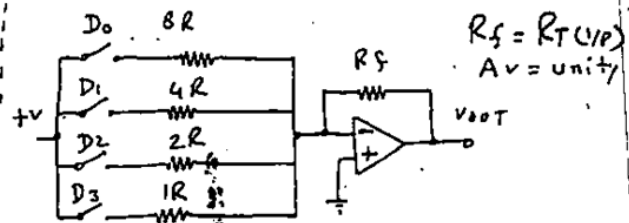

Binary weighted because

values of Resistor at  $V_p$  ratio same as Binary weight but invert to  $V_p$  bit number.

$$V_o = \left( \frac{R_f}{R_{in}} \right) V_{in}$$

